 


Kaitlyn Stumpf
 February 21st, 2016
 CSC 270, Spring
 Dominique Thiebaut

Homework #4 Problem 1

- Using as few additional gates as possible, implement the function $f(A, B, C, D)$ whose Karnaugh map is shown below, on the left, using the multiplexer shown on the right.

AB CD	00	01	11	10
00	1			1
01		1	1	
11		1	1	
10	1			1




My work for part one of problem 1 is shown below. For each CD row I connected the C & D binary value to its matching f (i.e. 11 maps to f_3), and set the input to be the defining feature of that row of the Karnaugh map.

CD AB	00	01	11	10
00	1			1
01		1	1	
11		1	1	
10	1			1

When $c=0$ & $d=0$, ($00=f_0$), \bar{b} .
 When $c=0$ & $d=1$, ($01=f_1$), b .
 When $c=1$ & $d=1$, ($11=f_3$), b .
 When $c=1$ & $d=0$, ($10=f_2$), \bar{b} .

- Using as few additional gates as possible, implement the function $g(A, B, C, D)$ whose Karnaugh map is shown below, on the left, using the multiplexer shown on the right.

AB \ CD	00	01	11	10
00	1		1	1
01	1	1	1	
11	1	1	1	
10	1		1	1

 

My work for part one of problem 1 is shown below. For each CD row I connected the C & D binary value to its matching f (i.e. 11 maps to f_3), and set the input to be the defining feature of that row of the Karnaugh map.

Problem 1, Part 2

CD \ AB	00	01	11	10
00	1		1	1
01	1	1	1	
11	1	1	1	
10	1		1	1

When $A=0$ & $B=0$, ($00=f_0$), $g=1$.
 When $A=0$ & $B=1$, ($01=f_1$), $g=d$.
 When $A=1$ & $B=1$, ($11=f_3$), $g=1$.
 When $A=1$ & $B=0$, ($10=f_2$), $g=\bar{d}$.

Problem 2

Implement your two answers for Problem 1 in Python, and shown that your design is correct (although it might not be as minimal as required).

Your Python code should have the following features:

- It must contain a header with your name(s), and a description of what it does
- It must contain a mux() function with 6 inputs (A, B, C, D, C1, C0), and returning one value (Y).
- It must generate the truth table for f and for g.

Include the code and a copy of the output in your pdf. Please use a non-proportional font when displaying code and output: it makes it much easier for the reader to read and understand code quickly.

CODE:

```
# Kaitlyn Stumpf
# Feb 23, 2016
# CSC270, Thiebaut
# Hw4, Python/Java Ques.

# This program contains a mux() func w/ 6 inputs (F0, F1, F2, F3, C1, C0)
# that returns one value (Y).
# It prints out truth tables for my two answers for Prob 1,
# by calling the mux() function w/ the values specific to the problem.

def mux(F0, F1, F2, F3, C1, C0):
    """
    Gets F0, F1, F2, F3 input values as well as C1 and C0.
    Combines C1 & C0 into a binary string & then into a base ten value.
    Uses base ten value to pick which of the multiplexer inputs, f0, f1,
    f2, or f3,
    is needed, and returns this vale.
    """
    muxInputs = [F0, F1, F2, F3]
    Y = 0
    # Assuming inputs to C1 & C0 are ints equal to either 0 or 1, turns
    into binary string.
    binaryStr = str(C1) + str(C0)
    # Then converts binary string into base ten int.
    baseTenVal = int(binaryStr, 2)

    return muxInputs[baseTenVal]

def truthTable():
    """ truthTable() references mux() in order to print a truth table
    for the multiplexers f & g.
    """

    print
    print( " For the following multiplexer: ")
    print( " F0 = B', F1 = B, F2 = B', F3 = B ")
```

```

print( " C1 = C, C0 = D ")
print( " Given this info, I generated the following truth table.")
print
print( "  A  B  C  D  |  f  " )
print( "-----+-----" )
for A in [0, 1]:
    for B in [0, 1]:
        BINV = 0
        if B == 0:
            BINV = 1
        for C in [0, 1]:
            for D in [0, 1]:
                f = mux(BINV, B, BINV, B, C, D)
                print("  {0}  {1}  {2}  {3}  |  {4}

".format(A, B, C, D, f))

print
print
print( " For the following multiplexer: ")
print( " F0 = 1, F1 = D, F2 = D', F3 = 1 ")
print( " C1 = A, C0 = B ")
print( " Given this info, I generated the following truth table.")
print
print( "  A  B  C  D  |  g  " )
print( "-----+-----" )
for A in [0, 1]:
    for B in [0, 1]:
        for C in [0, 1]:
            for D in [0, 1]:
                DINV = 0
                if D == 0:
                    DINV = 1
                g = mux(1, D, DINV, 1, A, B)
                print("  {0}  {1}  {2}  {3}  |

{4} ".format(A, B, C, D, g))

def main():
    ''' Calls truthTable in order to print the truth table.'''
    truthTable()

main()

```

OUTPUT:

Kaitlyns-MacBook-Pro:hw4 kaitlynstumpf\$ python stumpf_hw4.py

```

For the following multiplexer:
F0 = B', F1 = B, F2 = B', F3 = B
C1 = C, C0 = D
Given this info, I generated the following truth table.

```

A	B	C	D	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0

0	1	0	1		1
0	1	1	0		0
0	1	1	1		1
1	0	0	0		1
1	0	0	1		0
1	0	1	0		1
1	0	1	1		0
1	1	0	0		0
1	1	0	1		1
1	1	1	0		0
1	1	1	1		1

For the following multiplexer:

$F_0 = 1, F_1 = D, F_2 = D', F_3 = 1$

$C_1 = A, C_0 = B$

Given this info, I generated the following truth table.


A	B	C	D		g
0	0	0	0		1
0	0	0	1		1
0	0	1	0		1
0	0	1	1		1
0	1	0	0		0
0	1	0	1		1
0	1	1	0		0
0	1	1	1		1
1	0	0	0		1
1	0	0	1		0
1	0	1	0		1
1	0	1	1		0
1	1	0	0		1
1	1	0	1		1
1	1	1	0		1
1	1	1	1		1

Problem 3

Is the circuit below a latch? Why or why not?

If you find out that it is a latch, you should be able to indicate:

 - What are the inputs that are "passing" and putting the latch in a stable state.
- What input (S or R) must be activated (and how) to force a 1 on Q_i
- What input (S or R) must be activated (and how) to force a 0 on Q_i




To solve this problem, I first tested if the circuit above was a latch. I did this test by using a state table to test if changes in S and R caused Q_i and Q_j to change in a predictable way. If they changed in a predictable way, (i.e. whenever S and R switched values, Q_i and Q_j switched values as well), this would indicate that the values of S and R were being stored and remembered. My state table is found below.

S	R	Q_i	Q_j	Is Circuit Consistent?
0	1	1	1	0 Yes
0	1	1	1	0 Yes
1	0	0	0	1 Yes
1	0	0	0	1 Yes
1	0	0	0	1 Yes
0	1	0	0	0 No

I have used the state table above to prove by contradiction that this circuit is inconsistent, and therefore not a latch. It does not always properly switch off the values saved in Q_i and Q_j when S and R switch values. When the latch goes from $S = 1, R = 0$ to $S = 0, R = 1$, rather than Q_i and Q_j switching values (and thus properly remembering which value was passed), it accidentally sets both Q_i and Q_j to zero.

Therefore, the above circuit is not a latch.


Problem 4

 

- Can a latch be created with the upper of the two circuits above (AND with one inverted input)? You can use as many of these special ANDs as you need.
- Same question about the lower circuit (XOR with one inverted input)? You can use as many of these special XORs as you need.

- Please explain carefully why it is possible to create a latch, or why it is not possible to create a latch with each one the circuits.

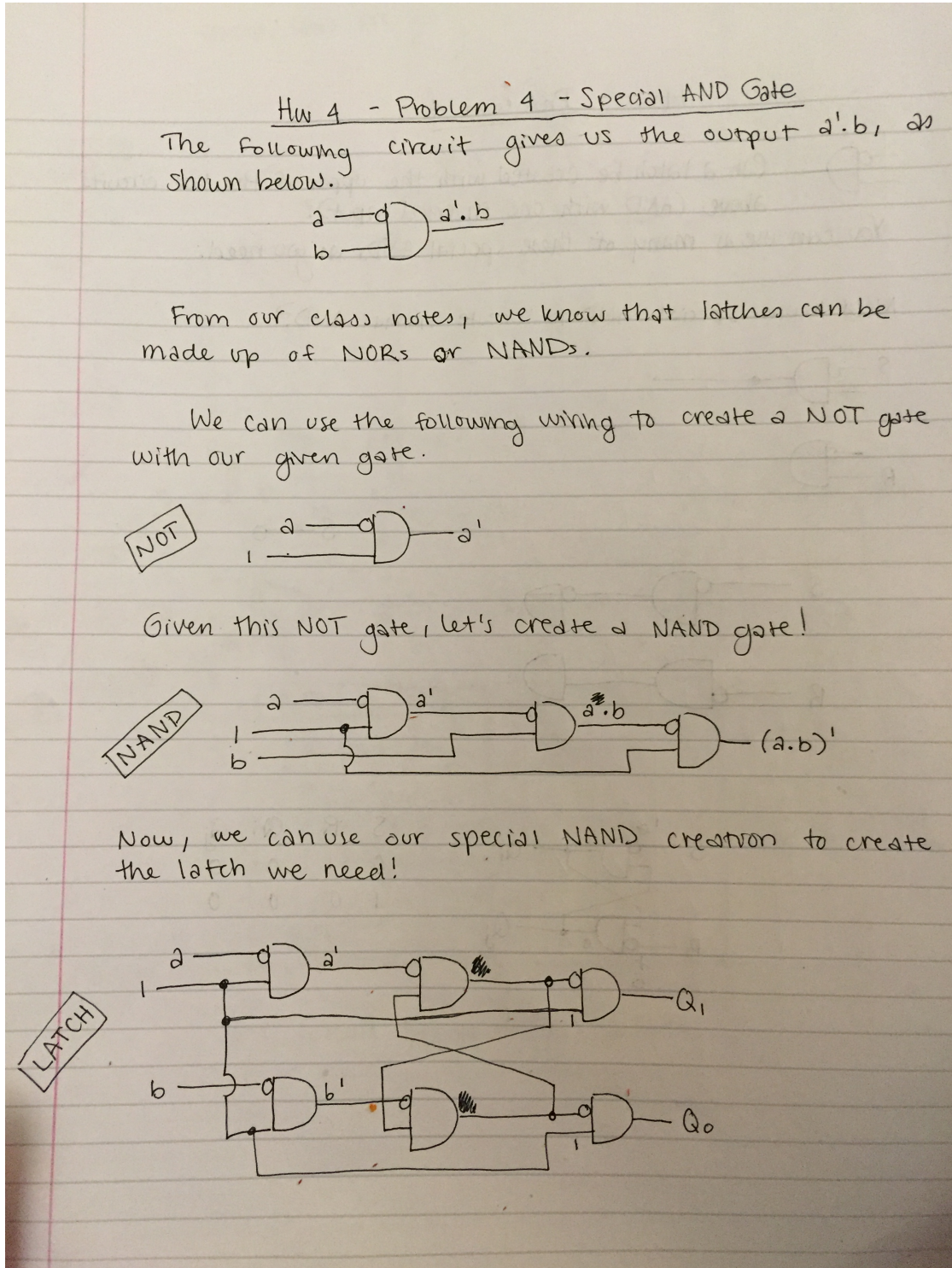I was confused about how to go about this question, and so I asked Karen Diaz for help! She guided me in how to think about the first part.



The special XOR gate with one inverted input, however, cannot be a latch. This is because, as proven in homework 2, the special XOR gate with one inverted input is not a universal gate. As shown by the truth table below, there is no exclusivity in the output of the special gate. This means that we cannot isolate a single a or b value and use this to build a universal gate.

a	b	$a \oplus b'$
0	0	1
0	1	0
1	0	0
1	1	1

Because we cannot use this special gate as a universal gate, it follows that it would not be possible to build either a NAND or a NOR gate using the special gate. Therefore, it would not be possible to build a latch using the special gate.